

# Computer Organization and Architecture Laboratory

## Assignment 3 (Verilog)

Group 63:

Pranav Nyati - 20CS30037

Shreyas Jena - 20CS30049

---

### Part 1:

Design of Ripple Carry Adders for 8, 16, 32, and 64 bits:

#### (a) Half Adder:

- **Inputs:** in1 and in2 (both are 1 bit inputs)
- **Outputs:** sum bit and c\_out bit (carry out)
- **Truth Table:**

Inputs		Outputs	
in1	in2	sum	c_out
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$\text{Sum} = \text{in1 XOR in2}; \quad \text{c\_out} = \text{in1 AND in2}$$

- **Figure:**

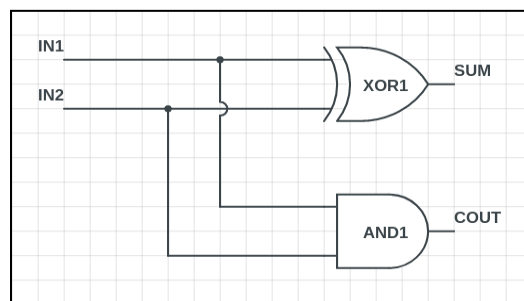


Fig 1. Logic Diagram of Half Adder


**(b) Full Adder:**

- **Inputs:** in1, in2, c\_in (all are 1 bit)
- **Outputs:** sum bit and c\_out bit
- **Truth Table:**

Inputs			Outputs	
in1	in2	c_in	sum	c_out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

**Sum = in1 XOR in2 XOR c\_in;**

**c\_out = (in1 AND in2) OR (in1 AND c\_in) OR (in2 AND c\_in)**

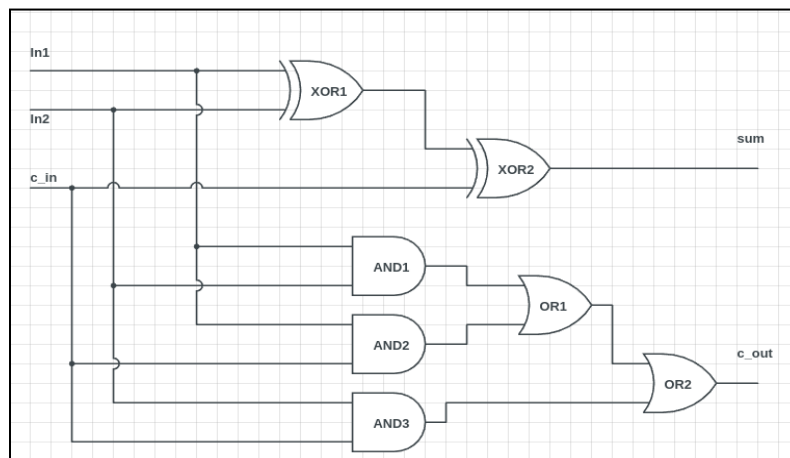

**Fig 2. Logic Diagram of Full Adder**

### (c) Ripple Carry Adder (RCA):

We can create a 8-bit RCA by cascading 8 full adder circuits into a single circuit. Similarly, we can create a 16-bit RCA by cascading two 8-bit RCA modules, a 32-bit RCA by cascading two 16-bit RCA modules, and a 64-bit RCA by cascading two 32-bit RCA modules.

- **8-bit RCA:**

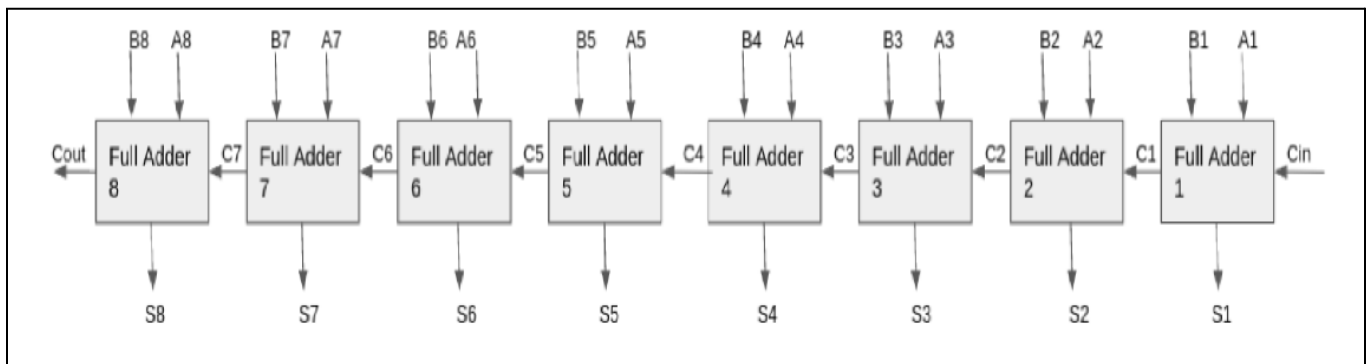


Fig 3. Logic Diagram of 8-bit RCA using 8 full adders in a cascading manner

- **16-bit RCA:**

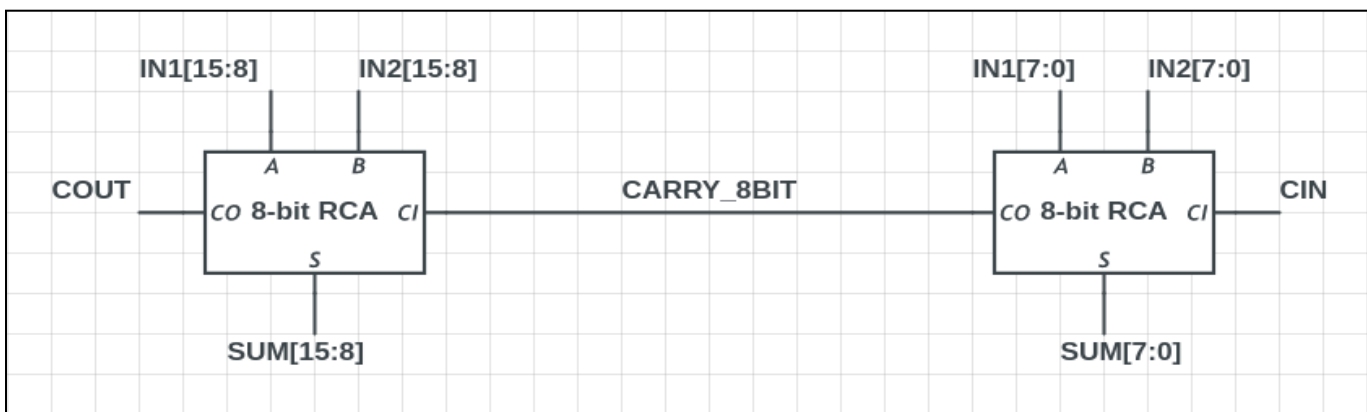


Fig 4. Logic Diagram of 16-bit RCA using two 8-bit RCA in succession

- **32-bit RCA:**

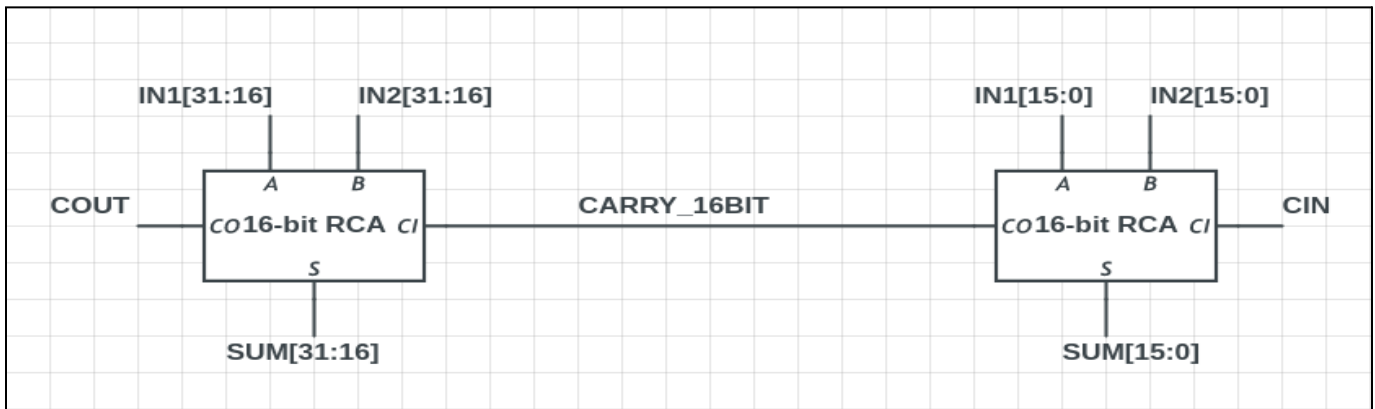


Fig 5. Logic Diagram of 32-bit RCA using two 16-bit RCA in succession

- **64-bit RCA:**

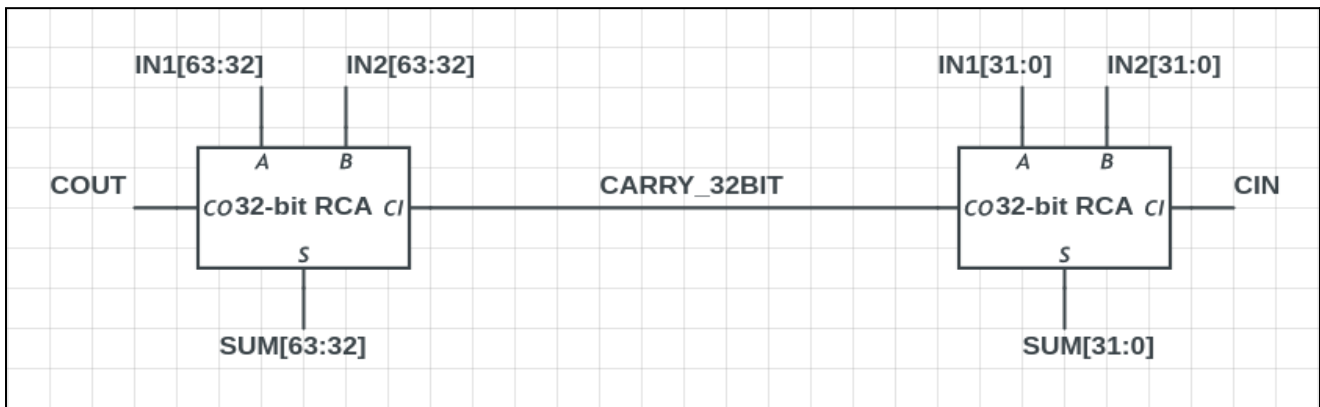


Fig 6. Logic Diagram of 64-bit RCA using two 32-bit RCA in succession

## TIME DELAYS:

### Observed longest timing delays:

- **8-bit RCA:**            **3.471ns** (0.497ns logic, 2.974ns route)
- **16-bit RCA:**        **6.167ns** (0.993ns logic, 5.174ns route)
- **32-bit RCA:**        **11.559ns** (1.985ns logic, 9.574ns route)
- **64-bit RCA:**        **22.343ns** (3.969ns logic, 18.374ns route)

**(d) How can you use the above circuit, to compute the difference between two n-bit numbers?**

**Soln:-**

An n-bit RCA in a general case takes two inputs in1 and in2 with the carry-in bit = 0, and calculates the sum  $in1 + in2$ . In order to calculate the difference of two n-bit numbers  $in1 - in2$  (let us assume that  $in1 > in2$ ), we can pass the first n-bit number as in1, the 2nd n-bit number as 1's complement of in\_2 (i.e, do bit wise complement of each bit in in2, and pass this 1's complement as in\_2), and the initial carry\_in bit as 1.

The result will be:

$$\begin{aligned} \text{Res} &= (in1 + 1's \text{ complement of } in2 + 1) \\ &= (in1 + (1's \text{ complement of } in2 + 1)) \\ &= (in1 + 2's \text{ complement of } in2) \\ &= (in1 + (-in2)) \\ &= (in1 - in2) \end{aligned}$$

---